Making · L9 · Guide

Lesson plan and safety notes

For your parent or guide · 1 page

Goal

Explain why an LED only works one way round, and build a switched LED circuit.

- Use 2 × AA batteries.
- Add a resistor if using more than 3 V.