Making · L9 · Worksheet

LED and switch build card

1 page

Name _____ Date _____

Build

1. Battery + to the switch.
2. Switch to the LED’s long leg.
3. LED’s short leg back to battery –.
4. Press the switch. Does it light?
5. Turn the LED round. What happens?

1 Draw your circuit and label + and –.