
Making · L9 · Worksheet

Circuit tracing sheet

1 page

Name _____ Date _____

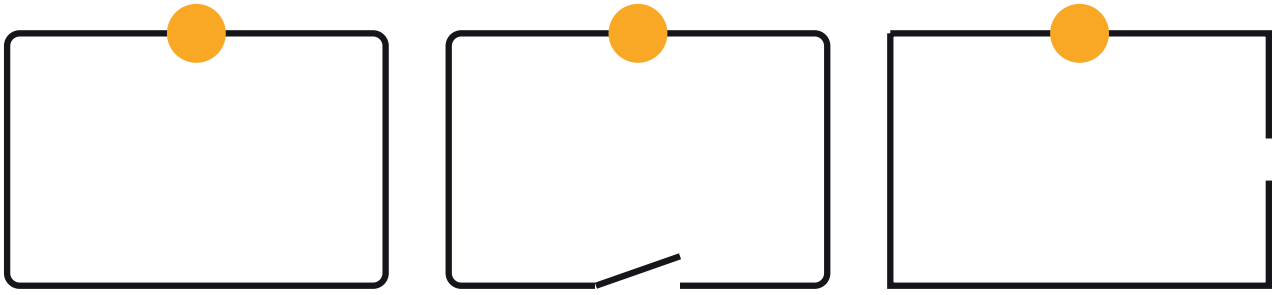Trace each circuit with your finger from the + of the battery. If you have to jump a gap, it's open.



A

B: switch open

C

Circuit	Open or closed?	Where is the gap?
A		
B		
C		

1. Draw a circuit with a battery, a bulb and a switch. Mark where the switch breaks the loop.